
 
 
 


1/1/123


Unit - 4INTRODUCTION TO SEQUENTIAL LOGIC DESIGN* Sequential Circuits

 1 bit memory cell / cross coupled inverter / latch.



Drawback :- No provision to enter the required digital data

* S-R Flip-Flop (Set-Reset)

 


S	R	Clk	\bar{Q}_n	Q_{n+1}	\bar{Q}_{n+1}	
0	0	0	1	0	1	{ no change
0	0	1	0	1	0	
0	1	0	1	0	1	{ Reset
0	1	1	0	0	1	
1	0	0	1	1	0	{ set
1	0	1	0	1	0	
1	1	0	1	1	0	{ not allowed
1	1	1	0	1	0	race around condn

Case I

$$① S=0, R=0, Q_n=0, \bar{Q}_n=1$$

$$Q_{n+1} = , \bar{Q}_{n+1} =$$

* Clock S-R Flip Flop

 


Clock	S	R	Q_{n+1}	\bar{Q}_{n+1}
1	0	0	Q_n	\bar{Q}_n
1	0	1	0	1
1	1	0	1	0
1	1	1	?	?


* S-R Flip Flop with Preset and Clear

Preset \rightarrow resets FF

Clear \rightarrow Set FF

 

Block diagram:-

 




As Preset and Clear are active low for normal working of the flip flop this two should be connected to V_{cc}


If preset is active i.e. if it is zero then flip flop will clear and if clear is active then FF will clear

Inputs

CLK	Pr	Cr	O/P	Operation performed
1	1	1	SR FF TT	Normal FF
0	1	0	0	clear
0	0	1	1	set

* J K Flip Flop :-

 

 


J_n	K_n	Q_n	\bar{Q}_n	S_n	R_n	Q_{n+1}	\bar{Q}_{n+1}
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	0	1
1	0	0	1	1	0	0	1
1	0	1	0	0	0	0	1
1	1	0	1	1	0	1	0
1	1	1	0	0	1	0	1

Not allowed


Reduced table

J_n	K_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

* Master-Slave JK-FF

 


Edge triggered

 

they are +ve &


Level triggered

 

latch

Circuit changes its state at high level and low level that is level.


- Symbol of Master slave JK-FF

 

(uM) * Toggle Flip Flop - (T FF)

whenever $J = K$

Symbol:-

 


Truth Table -

IC - 7476

Input	Output
T _n	Q _{n+1}
0	Q _n
1	Q̄ _n

If $T = 1$, T FF acts as Toggle switch
i.e. for every clock pulse output changes.

* DFF - Delay Flip Flop

 

In Delay FF the input data appears at the output at the end of the clock pulse.
i.e. the transfer of data from I/p to O/p is delayed and, hence the name is DFF.

I/P	O/P
D _n	Q _{n+1}
0	0
1	1

Imp

* Excitation table of Flip Flops

Present state	Next state	SRFF	JK FF	T FF	D FF
Q_n	Q_{n+1}	S_n R_n	J_n K_n	T_n	D_n
0	0	0 X	0 X	0	0
0	1	1 0	1 0	1	1
1	0	0 1	0 1	1	0
1	1	X 0	X 0	0	1

* Application of flip flop


- 1) Registers - collection of flip flops

N bit register

N FF are required.

 
- 1) Serial in Serial out (CSISO)
- 2) Serial in Parallel out (SIPo)
- 3) Parallel in Serial out (PISO)
- 4) Parallel in Parallel out (PIPO)

* Serial in Serial out \rightarrow left shift



$C1k$	$Q_3 = D_3$	$Q_2 = D_2$	$Q_1 = D_1$	$Q_0 = D_0$	Din
↓	0	0	0	1	1
↓	0	0	1	0	1
↓	0	1	1	1	1
↓	1	1	1	1	1

* S I P O → Right shift.

 


Here, data is loaded bit by bit first fill the time outputs are disabled. As soon as loading is completed and all the flip flop contains the required data the outputs are enabled so that loaded data is made available over the all output lines simultaneously



* PISO

B₃

 


* PIPO

IMP

* 4 bit Ring Counter

 
- Q1 Draw and explain 4 bit Ring Counter
 Q2 with diagram explain working of -



Clk	Q_0	Q_1	Q_2	Q_3
X				
↓	1	0	0	0
↓	0	1	0	0
↓	0	0	1	0
↓	0	0	0	1

1 Pulse is being circulated

 * 4 bit Twisted Ring Counter / Johnson's Counter / Moebius



CLK $Q_0 \ Q_1 \ Q_2 \ Q_3$

\downarrow	0	0	0	0
\downarrow	1	0	0	0
\downarrow	1	1	0	0
\downarrow	1	1	1	0
\downarrow	1	1	1	1
\downarrow	0	1	1	1
\downarrow	0	0	1	1
\downarrow	0	0	0	1