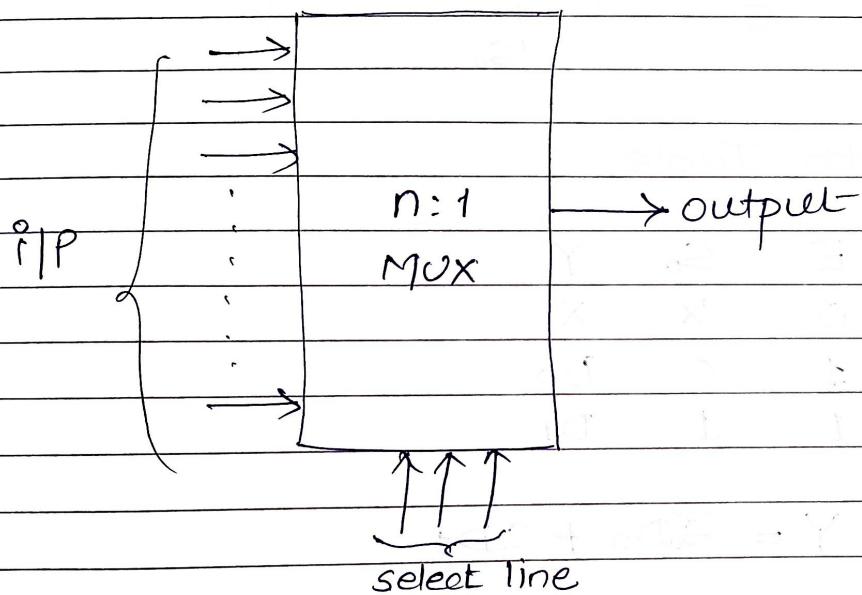


Multiplexer

Multiplexer is a combinational logic circuit having many inputs and one output.

Multiplexer is many to one.

In multiplexer select line select the one input as a output



Types of Multiplexer

1. 2:1 Multiplexer
2. 4:1 Multiplexer
3. 8:1 Multiplexer
4. 16:1 Multiplexer

Select lines

$$2^m = n$$


m = Select lines

2:1 Multiplexer

Inputs : 2

Output : 1

Select lines : 1

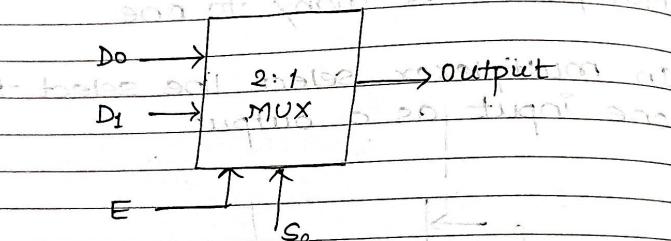


Truth Table

E	S_0	Y
0	X	X
1	0	D_0
1	1	D_1

$$Y = \bar{S}_0 D_0 + S_0 D_1$$

Circuit diagram

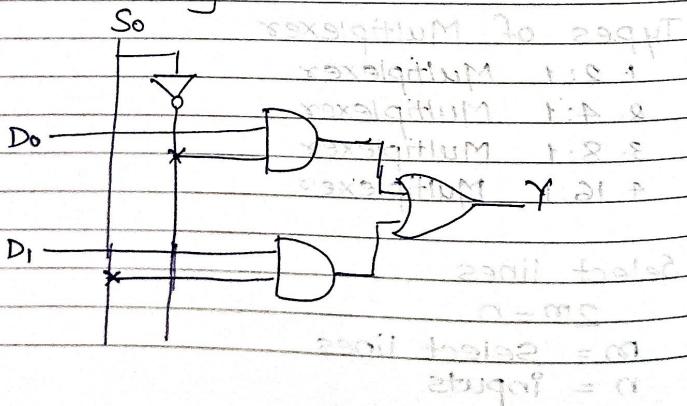


4:1 Multiplexer

Inputs : 4

Outputs : 1

Select lines : 2

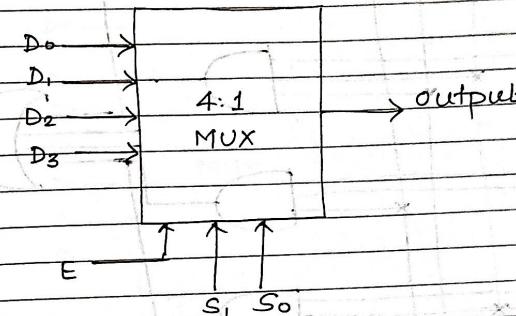


Truth Table

E	S_1	S_0	Y
0	X	X	X
1	0	0	D_0
1	0	1	D_1
1	1	0	D_2
1	1	1	D_3

Equation:

$$Y = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

Circuit diagram:

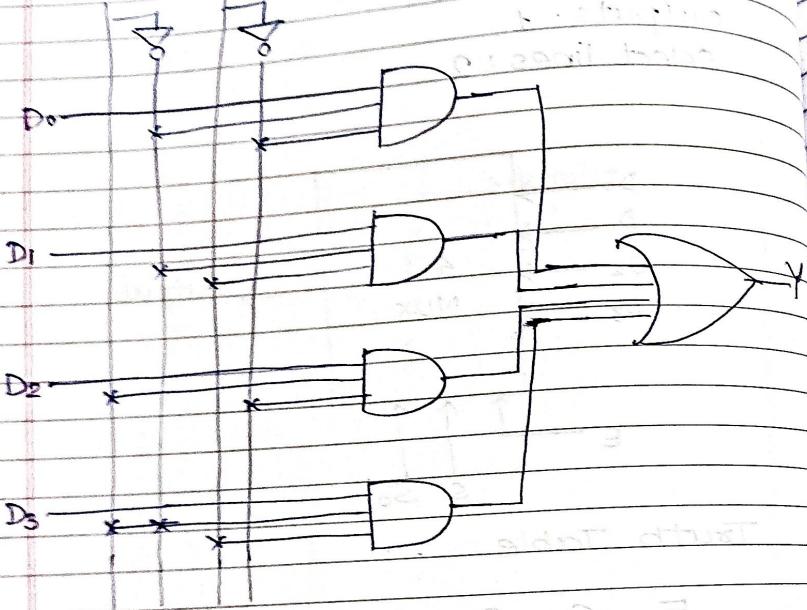

	Y	D ₀	D ₁	D ₂	E
00	X	X	X	0	0
01	0	0	0	1	1
10	1	0	0	1	0
11	0	1	0	1	1
12	1	1	0	1	1
13	0	1	1	1	0
14	1	0	1	1	1
15	0	0	1	1	0


$$D_0 + D_1S_2 + D_2S_1 + D_3S_0 = Y$$

8:1 Multiplexer

Inputs: 08

Outputs: 01

Select lines: 03

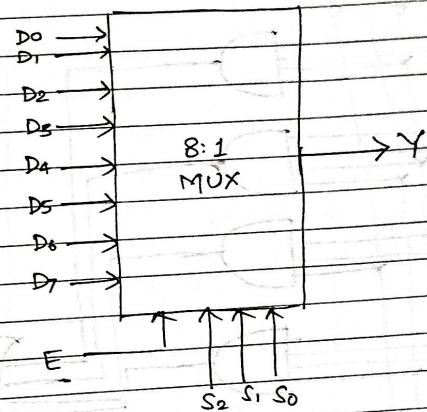


Truth Table

E	S ₂	S ₁	S ₀	Y
0	X	X	X	X
1	0	0	0	D ₀
1	0	0	1	D ₁
1	0	1	0	D ₂
1	0	1	1	D ₃
1	1	0	0	D ₄
1	1	0	1	D ₅
1	1	1	0	D ₆
1	1	1	1	D ₇


Equation:
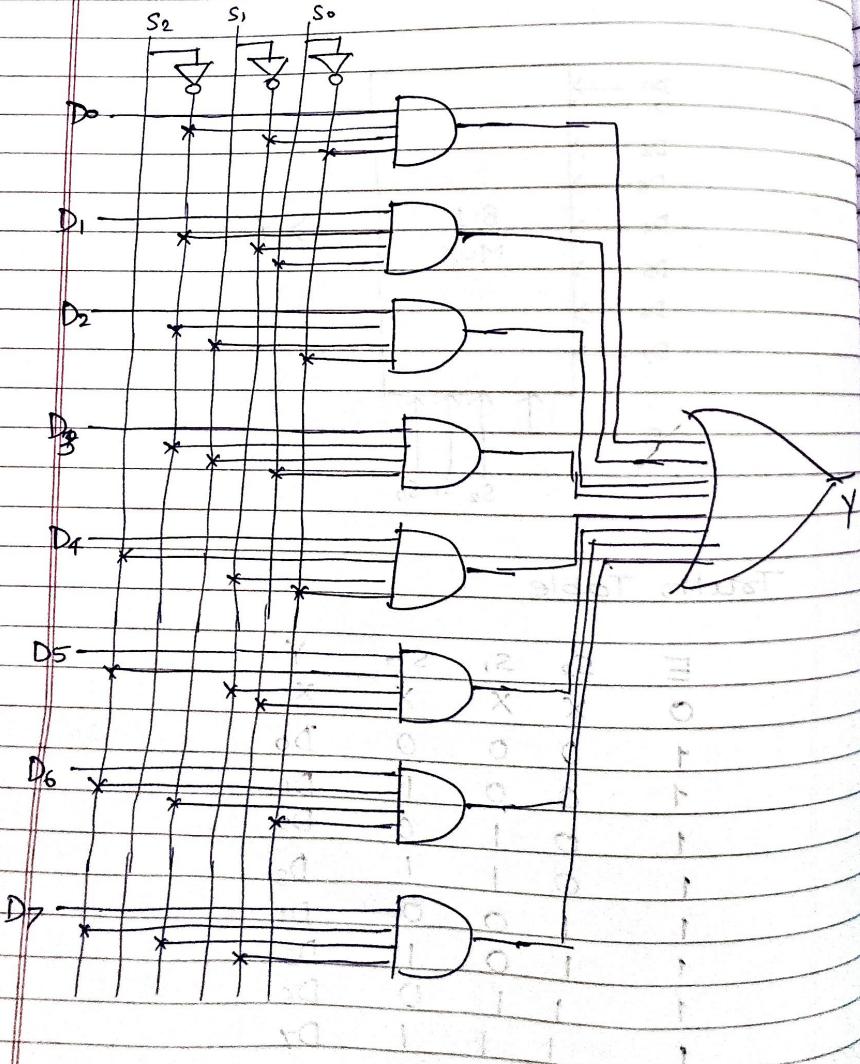
$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_2 \bar{S}_1 S_0 D_1 + \bar{S}_2 S_1 \bar{S}_0 D_2 + \\ \bar{S}_2 S_1 S_0 D_3 + S_2 \bar{S}_1 \bar{S}_0 D_4 + S_2 \bar{S}_1 S_0 D_5 + \\ S_2 S_1 \bar{S}_0 D_6 + S_2 S_1 S_0 D_7$$



Multiplexer as a function generator
Implement the following function using
8:1 Multiplexer.

$$F(a, b, c) = \sum m(3, 5, 6)$$

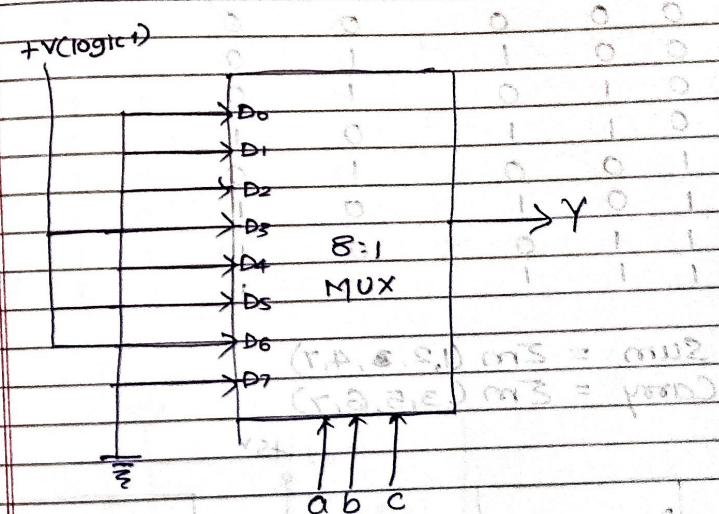


Implement full Adder using 8:1 MUX.

Truth Table:

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	XOR	XOR


$$\text{Sum} = \sum m(1, 2, 3, 4, 7)$$

$$\text{Carry} = \sum m(3, 5, 6, 7)$$

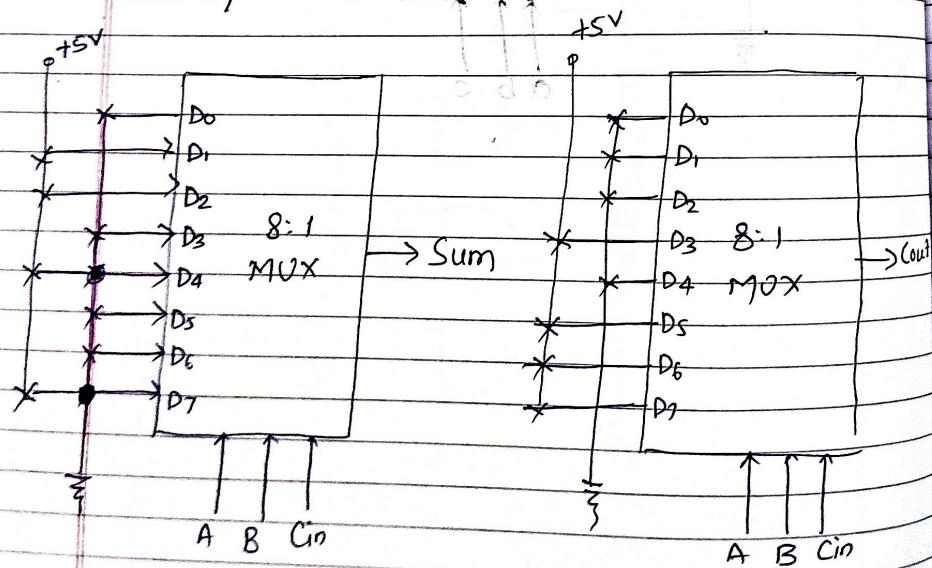

Implement following function using 4:1 MUX
 $F(A, B, C) = \sum m(1, 3, 5, 6)$

A	B	C	γ	γ	Output
0	0	0	0	0	C
0	0	1	1	1	C
0	1	0	0	0	C
0	1	1	1	1	C
1	0	0	0	0	C
1	0	1	1	1	C
1	1	0	1	0	\bar{C}
1	1	1	0	1	C

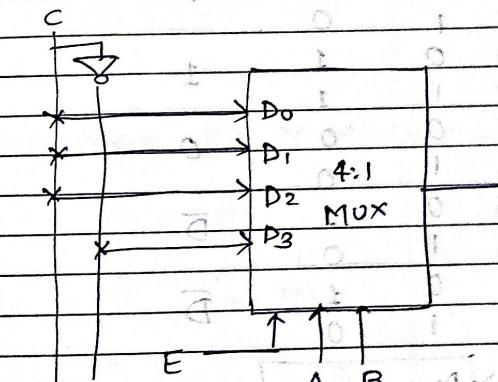


Implement expression using 8:1 MUX

$$F(A, B, C, D) = \Sigma m(0, 2, 3, 6, 8, 9, 12, 14)$$


Truth Table

A	B	C	D	Y	\bar{D}
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	1	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	0	1	0
1	0	0	1	1	1
1	0	1	0	0	*
1	0	1	1	0	*
1	1	0	0	1	0
1	1	0	1	0	*
1	1	1	0	1	0
1	1	1	1	0	*

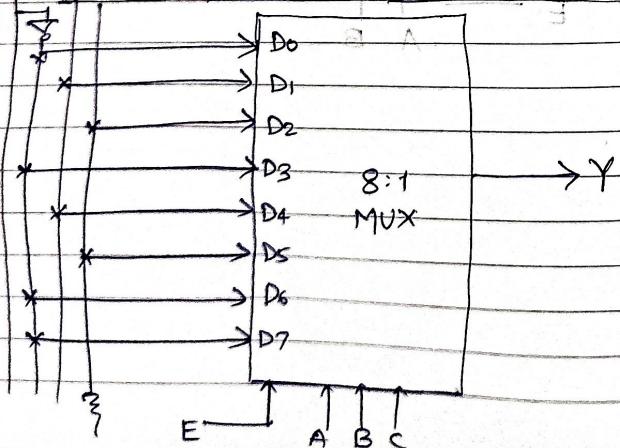


cascading Multiplexers


Implement 4:1 MUX using 2:1 MUX

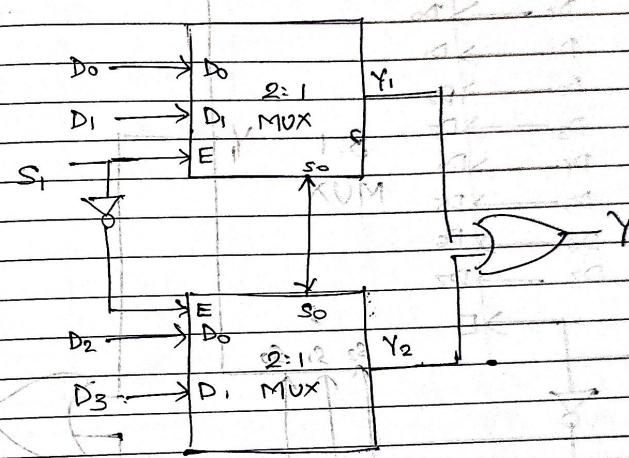


Implement 8:1 MUX using 4:1 MUX

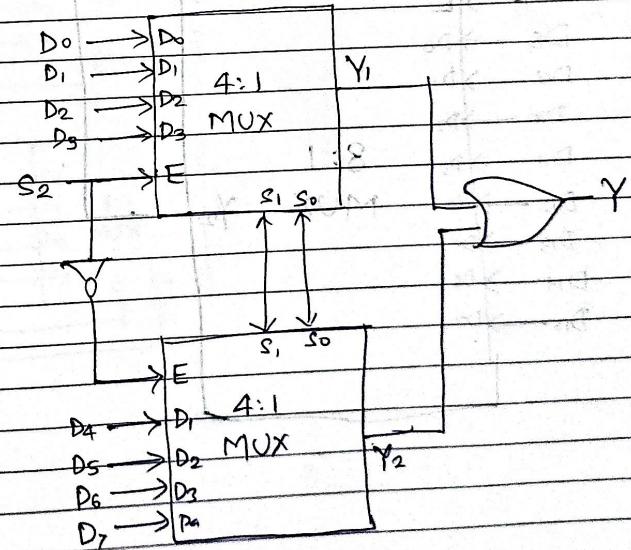

Implement 16:1 Multiplexer using 8:1 MUX

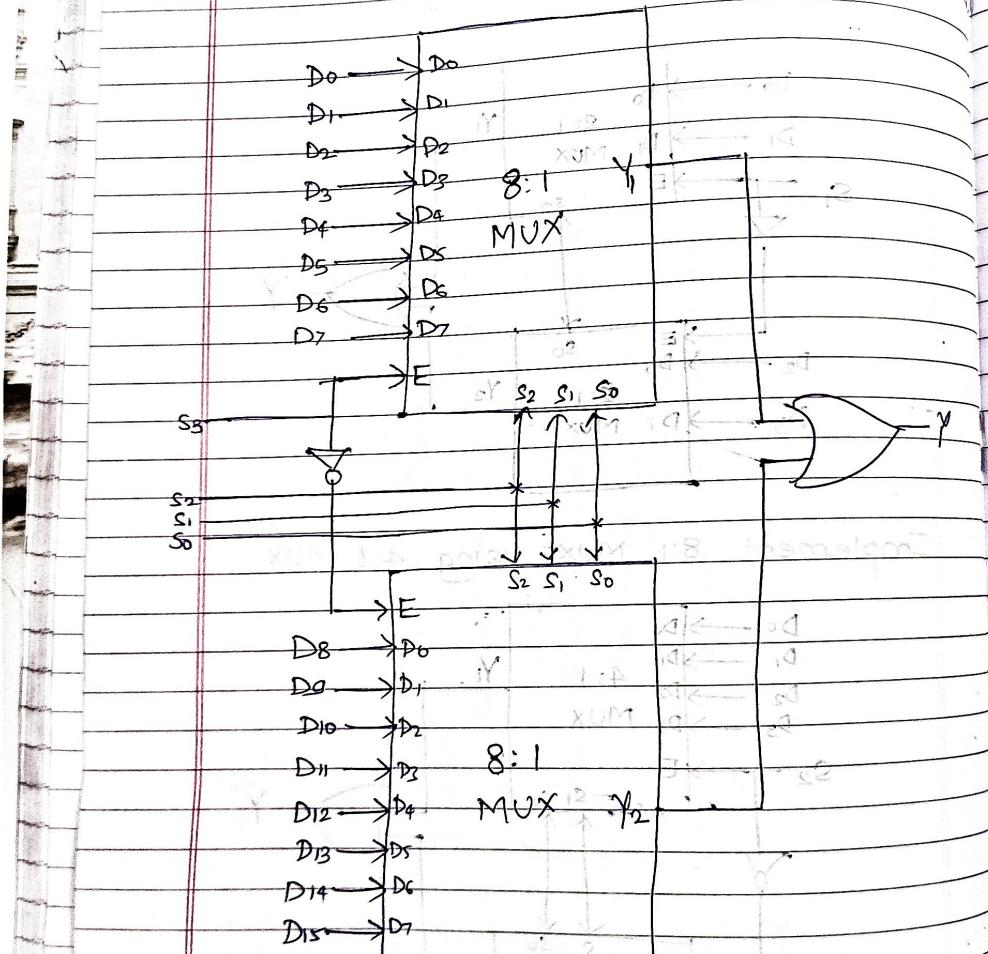

Design 16:1 Multiplexer using 4:1 MUX

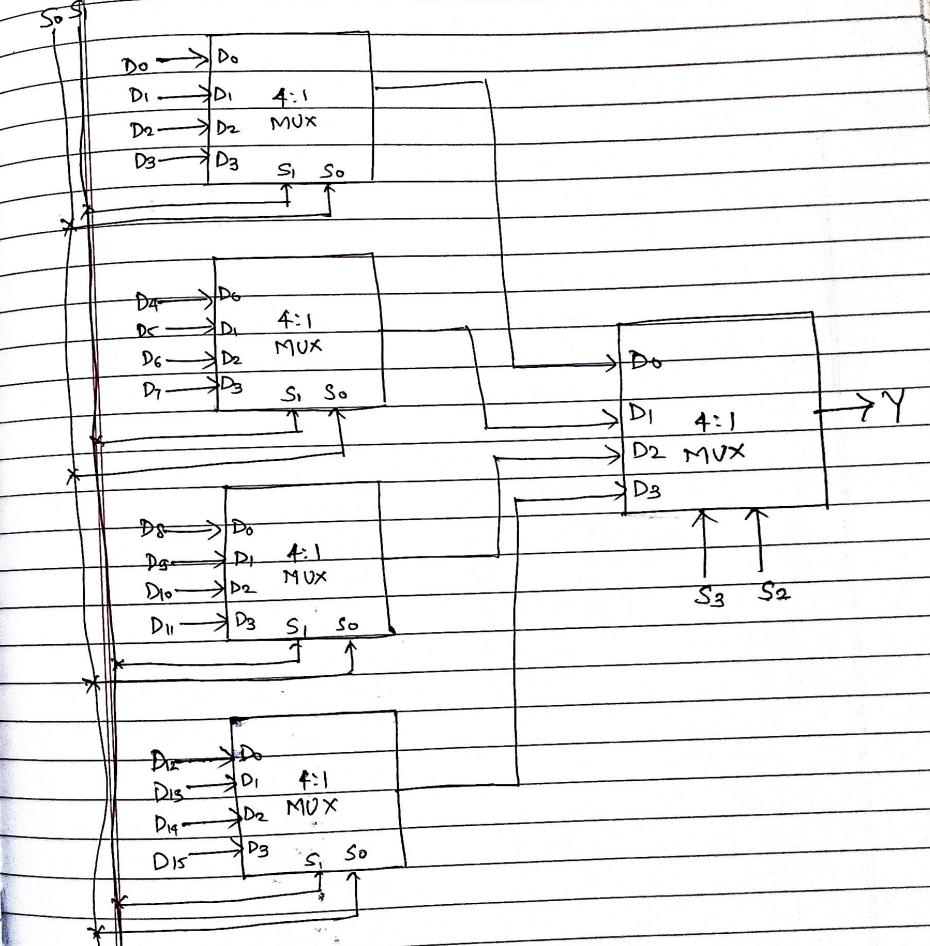

Implement function using 4:1 MUX


$$F(A, B, C) = \sum m(1, 3, 5, 6)$$

Implement function using 8:1 MUX

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 8, 9, 12, 14)$$

Demultiplexers

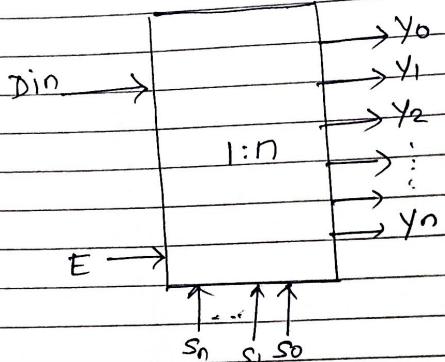Demultiplexer is one input and many output




Type of demultiplexers

1. 1:2 demultiplexer
2. 1:4 demultiplexer
3. 1:8 demultiplexer
4. 1:16 demultiplexer

1:2 Demultiplexer

input - one
output - two

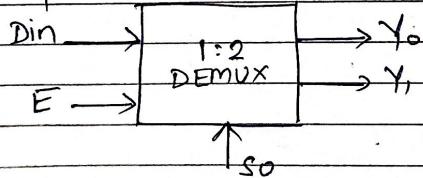


E	S0	Y0	Y1
0	X	0	0
1	0	Din	0
1	1	0	Din

The logical expression

$$Y_0 = S_0 \cdot D_{in}$$

$$Y_1 = S_0 \cdot D_{in}$$

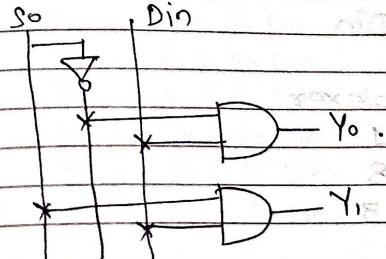


1:14 Demultiplexer

Inputs - 1

outputs - 4

Selecting - 2

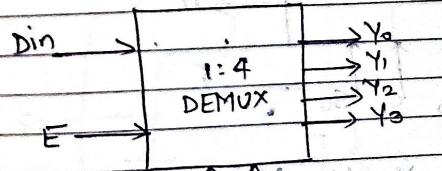

E	S1	S0	Y0	Y1	Y2	Y3
0	X	X	0	0	0	0
1	0	0	Din	0	0	0
1	0	1	0	Din	0	100
1	1	0	0	0	Din	100
1	1	1	1	0	0	Din

The logical expression of the term of Y

$$Y_0 = \bar{S}_1 \bar{S}_0 D_{in}$$

$$Y_1 = \bar{S}_1 S_0 D_{in}$$

$$Y_2 = S_1 \bar{S}_0 D_{in}$$


$$Y_3 = S_1 S_0 D_{in}$$

1:8 Demultiplexer

Inputs - 1

Outputs - 8

Select lines - 3

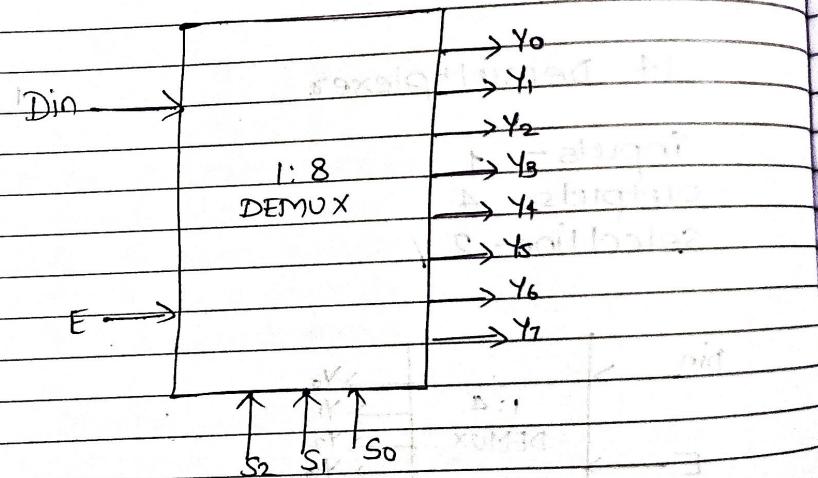

E	S_2	S_1	S_0	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
X	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	D_{in}	X	X					
1	0	0	1		D_{in}						
1	0	1	0			D_{in}					
1	0	1	1				D_{in}				
1	1	0	0					D_{in}			
1	1	0	1						D_{in}		
1	1	1	0							D_{in}	
1	1	1	1								D_{in}

logical Expression

$$Y_0 = \bar{S}_1 \bar{S}_0 D_{in}$$

$$Y_1 = \bar{S}_2 \bar{S}_1 S_0 D_{in}$$

$$Y_2 = \bar{S}_2 S_1 \bar{S}_0 D_{in}$$

$$Y_3 = \bar{S}_2 S_1 S_0 D_{in}$$


$$Y_4 = S_2 \bar{S}_1 \bar{S}_0 D_{in}$$

$$Y_5 = S_2 \bar{S}_1 S_0 D_{in}$$

$$Y_6 = S_2 S_1 \bar{S}_0 D_{in}$$

$$Y_7 = S_2 S_1 S_0 D_{in}$$

Design 1:8 demultiplexer using 1:4 demux

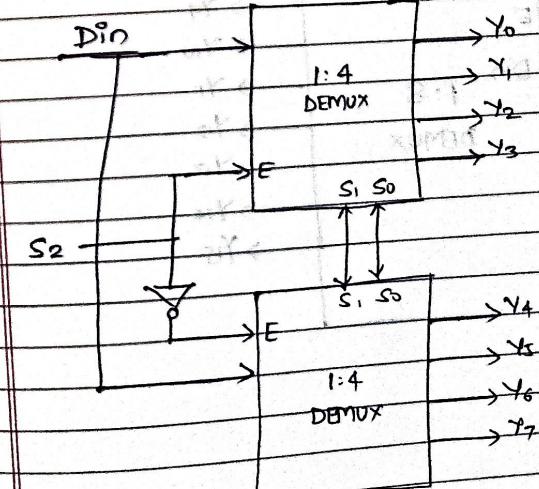

Design 1:16 demultiplexer using 1:8 Demux

